

# Control Systems

G V V Sharma\*

## CONTENTS

### 1 Feedback Circuits 1

**Abstract**—The objective of this manual is to introduce control system design at an elementary level.

Download python codes using

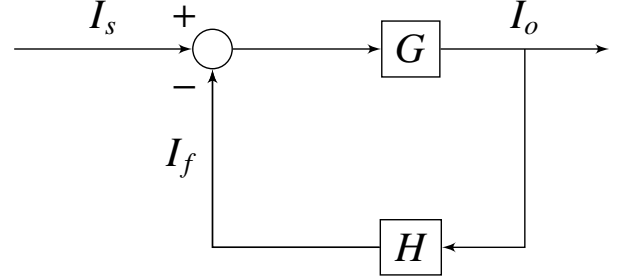


Fig. 1.0.2

### 1 FEEDBACK CIRCUITS

1.0.1. Consider a Feedback Current Amplifier formed by cascading an Inverting Opamp  $\mu$  with a MOSFET (NMOS). The output current is the Drain Current of the NMOS. Assume that Opamp has an input resistance  $R_{id}$ , an Open Circuit Voltage Gain  $\mu$ , and an output resistance  $r_{o1}$

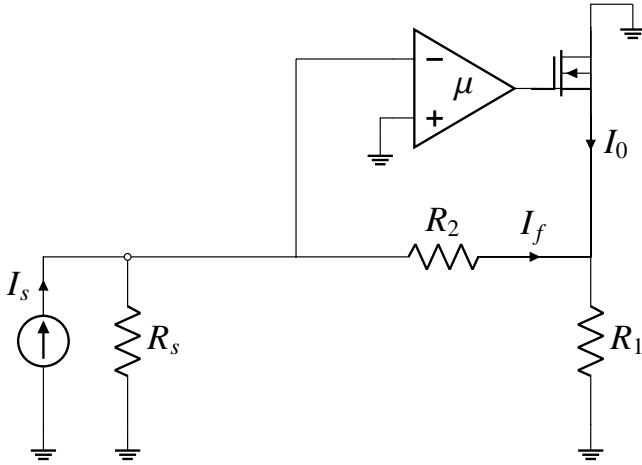


Fig. 1.0.1

1.0.2. Represent the Control System using a block diagram

**Solution:**

1.0.3. If loop gain is large, find approximate expression for closed loop gain  $T$

**Solution:** Given,

$$GH \gg 1 \quad (1.0.3.1)$$

$$T = \frac{G}{1 + GH} \simeq \frac{1}{H} \quad (1.0.3.2)$$

$$H = \frac{I_f}{I_o} = -\frac{R_1}{R_1 + R_2} \quad (1.0.3.3)$$

$$T \simeq \frac{1}{H} = -\left(1 + \frac{R_2}{R_1}\right) \quad (1.0.3.4)$$

1.0.4. Find the G Circuit i.e the Gain Circuit and approximate expressions for  $G$ ,  $R_i$ ,  $R_o$

**Solution:** By replacing the Opamp with its equivalent model we can get the G circuit

$$R_i = R_s \parallel R_{id} \parallel (R_1 + R_2) \quad (1.0.4.1)$$

$$V_i = I_i R_i \quad (1.0.4.2)$$

$$I_o = -\mu V_i \frac{1}{1/g_m + (R_1 \parallel R_2 \parallel r_{o2})} \frac{r_{o2}}{r_{o2} + (R_1 \parallel R_2)} \quad (1.0.4.3)$$

$$G = \frac{I_o}{I_i} = -\mu \frac{R_i}{1/g_m + (R_1 \parallel R_2 \parallel r_{o2})} \frac{r_{o2}}{r_{o2} + (R_1 \parallel R_2)} \quad (1.0.4.4)$$

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

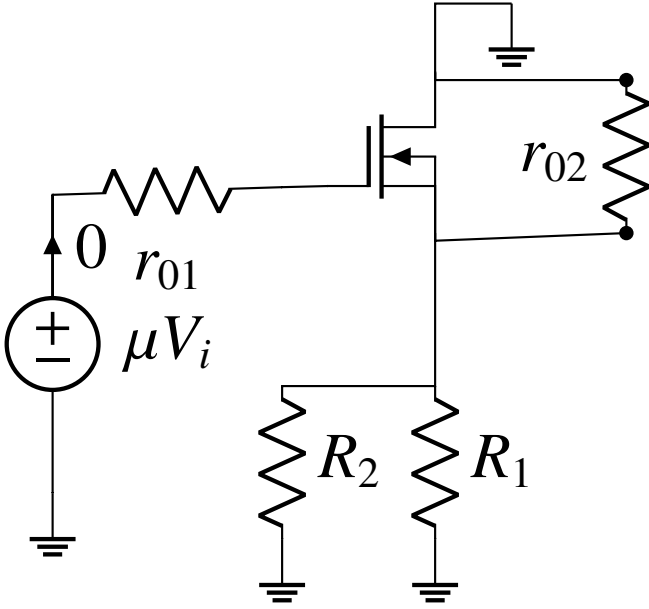


Fig. 1.0.4

We use the approximation

$$1/g_m \ll (R_1 || R_2 || r_{o2}) \quad (1.0.4.5)$$

This is because the  $\frac{1}{g_m}$  is in order of few  $\Omega$ s but,  $R_1$ ,  $R_2$  and  $r_{o2}$  are in order of  $k\Omega$ s

$$G = -\mu \frac{R_i}{R_1 || R_2} \quad (1.0.4.6)$$

$$R_o = r_{o2} + (R_1 || R_2) + (g_m r_{o2})(R_1 || R_2) \quad (1.0.4.7)$$

$$\Rightarrow R_o \approx g_m r_{o2} (R_1 || R_2) \quad (1.0.4.8)$$

1.0.5. Give expressions for  $GH$ ,  $T$ ,  $R_{if}$ ,  $R_{in}$ ,  $R_{of}$ ,  $R_{out}$

**Solution:**

$$GH = \mu \frac{R_i}{\frac{1}{g_m} + (R_1 || R_2 || r_{o2})} \frac{r_{o2}}{r_{o2} + (R_1 || R_2)} \frac{R_1}{R_1 + R_2} \quad (1.0.5.1)$$

Once again, using the approximation,

$$\Rightarrow GH \approx \mu \frac{R_i}{R_1 || R_2} \frac{R_1}{R_1 + R_2} = \mu \frac{R_i}{R_2} \quad (1.0.5.2)$$

For Input Resistance,

$$R_{if} = R_i / (1 + GH) \quad (1.0.5.3)$$

$$\Rightarrow \frac{1}{R_{if}} = \frac{1}{R_i} + \frac{\mu}{R_2} \quad (1.0.5.4)$$

$$\Rightarrow R_{if} = R_i || \frac{R_2}{\mu} \quad (1.0.5.5)$$

Substituting the value of  $R_i$ ,

$$R_{if} = R_s || R_{id} || (R_1 + R_2) || \frac{R_2}{\mu} \quad (1.0.5.6)$$

$$R_{if} = R_s || R_{in} \quad (1.0.5.7)$$

$$\Rightarrow R_{in} = R_{id} || (R_1 + R_2) || \frac{R_2}{\mu} \quad (1.0.5.8)$$

$$R_{in} \approx \frac{R_2}{\mu} \quad (1.0.5.9)$$

For Output Resistance,

$$R_{of} = R_o (1 + GH) \approx GHR_o \quad (1.0.5.10)$$

$$R_{of} \approx \mu \left( \frac{R_i}{R_2} \right) (g_m r_{o2}) (R_1 || R_2) \quad (1.0.5.11)$$

$$R_{out} = R_{of} = \mu \frac{R_i}{R_1 + R_2} (g_m r_{o2}) R_1 \quad (1.0.5.12)$$

1.0.6. Find numerical values for  $G$ ,  $H$ ,  $GH$ ,  $T$ ,  $R_i$ ,  $R_{if}$ ,  $R_{in}$ ,  $R_o$ ,  $R_{of}$ ,  $R_{out}$  given the following values  $\mu = 1000$ ,  $R_s = \infty$ ,  $R_{id} = \infty$ ,  $r_{o1} = 1 \text{ k}\Omega$ ,  $R_1 = 10 \text{ k}\Omega$ ,  $R_2 = 90 \text{ k}\Omega$

**Solution:** Using the given numerical values on the previously obtained equations, we obtain:

$$R_i = \infty || \infty || (10 + 90) = 100 \text{ k}\Omega \quad (1.0.6.1)$$

We can see that our approximation is valid

$$1/g_m = 0.2 \text{ k}\Omega \ll (10 || 90 || 20) \text{ k}\Omega = 6.2 \text{ k}\Omega \quad (1.0.6.2)$$

$$G = -1000 \frac{100}{10 || 90} = -11.11 \times 10^3 \quad (1.0.6.3)$$

$$H = -\frac{R_1}{R_1 + R_2} = -\frac{10}{10 + 90} = -0.1 \quad (1.0.6.4)$$

$$GH = 1111 \quad (1.0.6.5)$$

$$T \approx \frac{1}{H} = -\frac{1}{0.1} = -10 \quad (1.0.6.6)$$

$$R_{in} = \frac{R_2}{\mu} = \frac{90 \text{ k}\Omega}{1000} = 90 \Omega \quad (1.0.6.7)$$

$$R_o = g_m r_{o2}(R_1 \parallel R_2) = 5 \times 20(10 \parallel 90) = 900 k\Omega$$

(1.0.6.8)

$$R_{out} = (1 + GH)R_o = 1112 \times 900 \simeq 1000 M\Omega$$

(1.0.6.9)