

Control Systems

G V V Sharma*

CONTENTS

1 Feedback Circuits

1

Abstract—The objective of this manual is to introduce control system design at an elementary level.

Download python codes using

1 FEEDBACK CIRCUITS

1.0.1. Consider a Feedback Current Amplifier formed by cascading an Inverting Opamp μ with a MOSFET (NMOS). The output current is the Drain Current of the NMOS. Assume that Opamp has an input resistance R_{id} , an Open Circuit Voltage Gain μ , and an output resistance r_{o1}

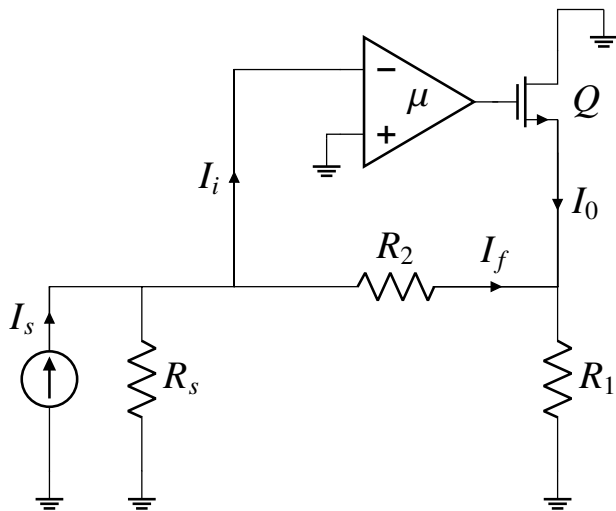


Fig. 1.0.1: Complete Circuit

1.0.2. Identify the type of Feedback Circuit and draw its corresponding Block Diagram Representation

Solution: The Feedback Circuit is a Shunt-Series Feedback Current Amplifier.

It is represented in a Feedback Block Diagram as follows

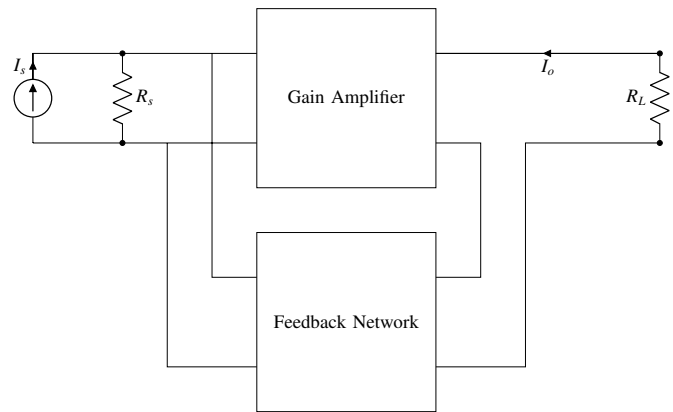


Fig. 1.0.2: Shunt Series Amplifier Block Diagram

1.0.3. Represent the Control System using a block diagram

Solution:

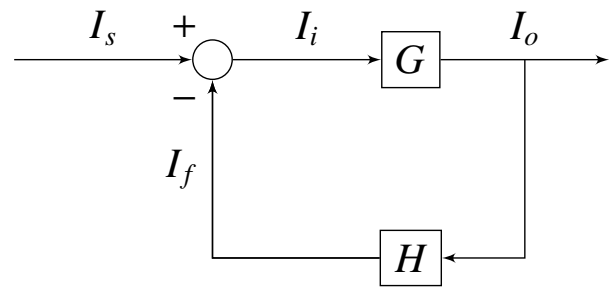


Fig. 1.0.3: Block Diagram

1.0.4. Represent the given circuit using a Small Signal Equivalent Model.

Solution: To draw Small Signal Equivalent model,

- Replace MOSFET with Current Source and Resistance in parallel with it.
- Replace Opamp with Voltage Source of the input Voltage multiplied by Gain

1.0.5. Describe the resistances involved in the circuit

Solution:

1.0.6. Draw the Block Diagram for the Gain Block, with the corresponding Circuit.

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

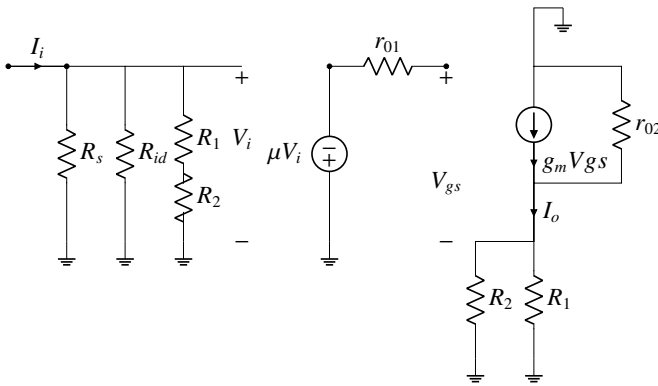


Fig. 1.0.4: Small Signal Model

Resistance	Description
R_{in}	Total Input Resistance
R_{out}	Total Output Resistance
R_{id}	Input resistance of Opamp
r_{o1}	Output resistance of Opamp
r_{o2}	Output resistance of MOSFET
R_i	Input resistance of Open Loop
R_o	Output resistance of Open Loop
R_{if}	Input resistance of Feedback
R_{of}	Output resistance of Feedback
R_s	Resistance of Current Source

TABLE 1.0.5

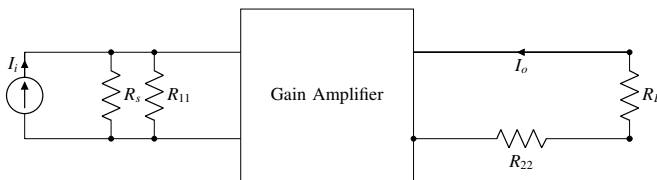
Solution:

Fig. 1.0.6: Gain Block

1.0.7. Calculate R_{11} and use it to find the Gain G.**Solution:** R_{11} is the resistance in parallel with the Resistance of the Source and the Input Impedance of the Opamp

$$R_{11} = R_1 + R_2 \quad (1.0.7.1)$$

$$R_i = R_s || R_{id} || (R_1 + R_2) \quad (1.0.7.2)$$

$$V_i = I_i R_i \quad (1.0.7.3)$$

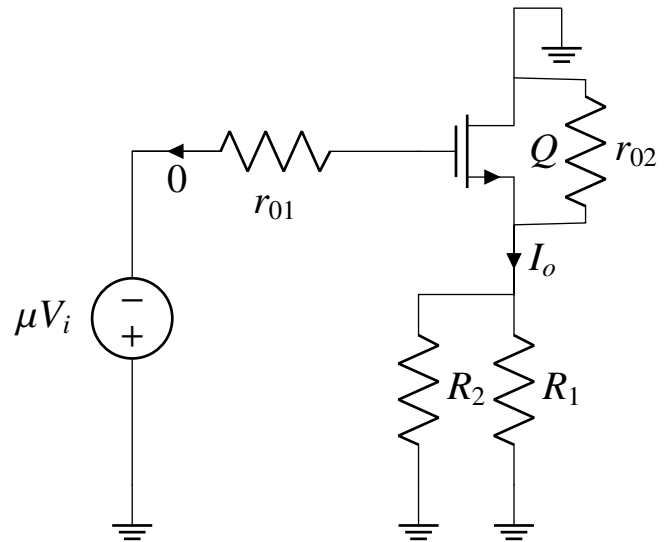


Fig. 1.0.6: Gain Circuit

$$I_o = -\mu V_i \frac{1}{1/g_m + (R_1 || R_2 || r_{o2})} \frac{r_{o2}}{r_{o2} + (R_1 || R_2)} \quad (1.0.7.4)$$

$$G = \frac{I_o}{I_i} = -\mu \frac{R_i}{1/g_m + (R_1 || R_2 || r_{o2})} \frac{r_{o2}}{r_{o2} + (R_1 || R_2)} \quad (1.0.7.5)$$

We use the approximation

$$1/g_m \ll (R_1 || R_2 || r_{o2}) \quad (1.0.7.6)$$

This is because the $\frac{1}{g_m}$ is in order of few Ω s but, R_1 , R_2 and r_{o2} are in order of k Ω s

$$G = -\mu \frac{R_i}{R_1 || R_2} \quad (1.0.7.7)$$

1.0.8. Draw the Block Diagram for the Feedback Block, with the corresponding Circuit.

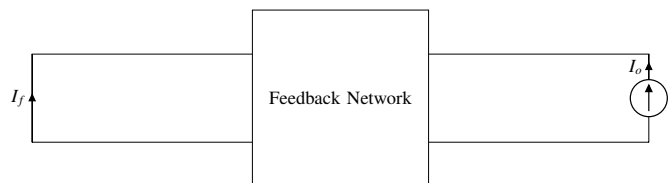
Solution:

Fig. 1.0.8: Feedback Block

1.0.9. Calculate R_{22} and use it to find the Feedback Gain H. **Solution:** From Feedback Circuit, R_{22} is resistance obtained by shorting Feedback Network

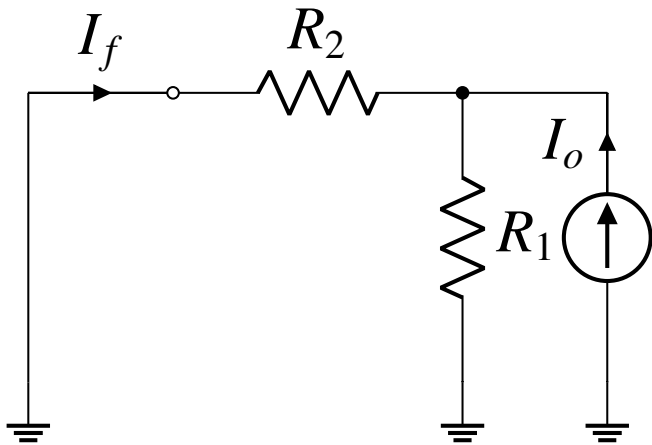


Fig. 1.0.8: Feedback Circuit

$$R_{22} = R_1 \parallel R_2$$

I_f is the current in R_2

$$\Rightarrow H = \frac{I_f}{I_o} = -\frac{R_1}{R_1 + R_2} \quad (1.0.9.2)$$

1.0.10. Calculate Loop Gain GH

Solution:

$$GH = \mu \frac{R_i}{\frac{1}{g_m} + (R_1 \parallel R_2 \parallel r_{o2})} \frac{r_{o2}}{r_{o2} + (R_1 \parallel R_2)} \frac{R_1}{R_1 + R_2} \quad (1.0.10.1)$$

$$\Rightarrow GH \simeq \mu \frac{R_i}{R_1 \parallel R_2} \frac{R_1}{R_1 + R_2} = \mu \frac{R_i}{R_2} \quad (1.0.10.2)$$

1.0.11. If loop gain is large, find approximate expression for closed loop gain T

Solution: Given,

$$GH \gg 1 \quad (1.0.11.1)$$

$$T = \frac{G}{1 + GH} \simeq \frac{1}{H} \quad (1.0.11.2)$$

$$T \simeq \frac{1}{H} = -\left(1 + \frac{R_2}{R_1}\right) \quad (1.0.11.3)$$

1.0.12. Give expressions for R_{if} , R_{in}

$$R_{if} = R_i / (1 + GH) \quad (1.0.12.1)$$

$$\Rightarrow \frac{1}{R_{if}} = \frac{1}{R_i} + \frac{\mu}{R_2} \quad (1.0.12.2)$$

$$\Rightarrow R_{if} = R_i \parallel \frac{R_2}{\mu} \quad (1.0.12.3)$$

Substituting the value of R_i ,

$$R_{if} = R_s \parallel R_{id} \parallel (R_1 + R_2) \parallel \frac{R_2}{\mu} \quad (1.0.12.4)$$

$$R_{if} = R_s \parallel R_{in} \quad (1.0.12.5)$$

$$\Rightarrow R_{in} = R_{id} \parallel (R_1 + R_2) \parallel \frac{R_2}{\mu} \quad (1.0.12.6)$$

$$R_{in} \simeq \frac{R_2}{\mu} \quad (1.0.12.7)$$

1.0.13. Give expressions for R_o , R_{of} , R_{out}

Solution:

$$R_o = r_{o2} + (R_1 \parallel R_2) + (g_m r_{o2})(R_1 \parallel R_2) \quad (1.0.13.1)$$

$$\Rightarrow R_o \simeq g_m r_{o2} (R_1 \parallel R_2) \quad (1.0.13.2)$$

$$R_{of} = R_o (1 + GH) \simeq GHR_o \quad (1.0.13.3)$$

$$R_{of} \simeq \mu \left(\frac{R_i}{R_2}\right) (g_m r_{o2}) (R_1 \parallel R_2) \quad (1.0.13.4)$$

$$R_{out} = R_{of} = \mu \frac{R_i}{R_1 + R_2} (g_m r_{o2}) R_1 \quad (1.0.13.5)$$

1.0.14. Given the following values

Parameter	Value
μ	1000
R_s	∞
R_{id}	∞
r_{o1}	$1k\Omega$
R_1	$10k\Omega$
R_2	$90k\Omega$
g_m	$5mA/V$
r_{o2}	$20k\Omega$

TABLE 1.0.14

Find numerical value of R_i and use it to find

the value of G

Solution: Using the given numerical values on the previously obtained equations, we obtain:

$$R_i = \infty \parallel \infty \parallel (10 + 90) = 100k\Omega \quad (1.0.14.1)$$

$$G = -1000 \frac{100}{10 \parallel 90} = -11.11 \times 10^3 \quad (1.0.14.2)$$

1.0.15. Check the validity of the approximation that we use to neglect $1/g_m$

Solution:

$$1/g_m = 0.2k\Omega \ll (10 \parallel 90 \parallel 20)k\Omega = 6.2k\Omega \quad (1.0.15.1)$$

Hence, we can see that our approximation is valid

1.0.16. Find the value of feedback gain H and open loop gain GH

Solution:

$$H = -\frac{R_1}{R_1 + R_2} = -\frac{10}{10 + 90} = -0.1 \quad (1.0.16.1)$$

$$GH = 1111 \gg 1 \quad (1.0.16.2)$$

1.0.17. Find the approximate value of closed loop gain T

Solution:

$$T \simeq \frac{1}{H} = -\frac{1}{0.1} = -10 \quad (1.0.17.1)$$

1.0.18. Find the values of R_{in} and R_{out}

Solution:

$$R_{in} = \frac{R_2}{\mu} = \frac{90k\Omega}{1000} = 90\Omega \quad (1.0.18.1)$$

$$R_o = g_m r_{o2} (R_1 \parallel R_2) = 5 \times 20(10 \parallel 90) = 900k\Omega \quad (1.0.18.2)$$

$$R_{out} = (1 + GH)R_o = 1112 \times 900 \simeq 1000M\Omega \quad (1.0.18.3)$$

1.0.19. Verify the above calculations using a Python code.

Solution:

```
codes/ee18btech11021/ee18btech11021_calc.py
```

Parameter	Value
R_i	$100k\Omega$
$1/g_m$	200Ω
G	-1.11×10^4
H	-0.1
GH	1111
T	-10
R_{in}	90Ω
R_o	$900k\Omega$
R_{out}	$1000M\Omega$

TABLE 1.0.18